

# **Application of Decoder, Encoder**

**By Engr. Rimsha**


# Combination Logic Implementation

- A **decoder** provides the  $2^n$  minterms of  $n$  input variables.
- Any **function** is can be expressed in **sum of minterms**.
- Use a decoder to make the minterms and an external OR gate to make the logical sum.
- In this way any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n$ -to- $2^n$  line decoder and  $m$  OR gates. Such implementation needs that the Boolean function is expressed in sum of minterms
- For example: consider a full adder.
  - $S(x,y,z) = \Sigma(1,2,4,7)$
  - $C(x,y,z) = \Sigma(3,5,6,7)$

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
 
# Implementation of Full Adder with a Decoder

- $S(x,y,z) = \Sigma(1,2,4,7)$
- $C(x,y,z) = \Sigma(3,5,6,7)$
- There are three inputs and eight outputs so we need 3-to-8-line decoder
- Two **OR** gates are required for logical **sum** of the desired minterms



## Implementation of Function with a Decoder Contd..

- $F_1(x,y,z) = \Sigma(0,1,3,5,6,7)$
- $F_2(x,y,z) = \Sigma(1,2,3,4,7)$


- A function with long list of minterms requires an OR gate with large number of inputs
- A function having a list of K minterms can be expressed in its **complemented** form  $F'$  with  $2^n - K$  minterms
- If the number of minterms in a function is greater than  $2^n/2$  then  $F'$  can be expressed with **fewer minterms**
- In such case it is advantageous to use a **NOR** gate to sum the minterms of  $F'$ . The output of the NOR gate **complements** this sum and generates the **normal** output  $F$



 
## Implementation of Function with a Decoder Contd..

- A function with long list of minterms requires an OR gate with large number of inputs
- A function having a list of K minterms can be expressed in its **complemented** form  $F'$  with  $2^n - K$  minterms
- If the number of minterms in a function is greater than  $2^n/2$  then  $F'$  can be expressed with **fewer minterms**
- In such case it is advantageous to use a **NOR** gate to sum the minterms of  $F'$ . The output of the NOR gate **complements** this sum and generates the **normal** output  $F$

- $F_1(x,y,z) = \Sigma(0,1,3,5,6,7)$
- $F_2(x,y,z) = \Sigma(1,2,3,4,7)$




 - $F_1'(x,y,z) = \Sigma(2,4)$
- $F_2'(x,y,z) = \Sigma(0,5,6)$


 
# Practice Problems

P1 : Consider the following circuit with an active high output decoder. Draw a truth table for  $X$  and  $Y$  in terms of  $a$ ,  $b$  and  $c$




# Practice Problems Contd..

We wish to design a decoder, with three inputs,  $x, y, z$ , and eight active high outputs, labeled  $0, 1, 2, 3, 4, 5, 6, 7$ . There is no enable input required. (For example, if  $xyz = 011$ , then output 3 would be 1 and all other outputs would be 0.)

The **only** building block is a two-input, four-output decoder (with an active high enable), the truth table for which is shown below.

P2


EN	A	B	0	1	2	3
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

Draw a block diagram of the system using as many of these building blocks as are needed.
 
# Encoders

- An **encoder** is a digital circuit that performs the **inverse operation** of a **decoder**.
- An encoder has  $2^n$  (or fewer) **input** lines and **n** **output** lines.
- The output lines generate the **binary code** corresponding to the input value





End of Lecture