

# Computer Architecture and Logic Design


## Magnitude Comparator, Decoder Circuit, Types, Its Application

Instructor Name: Engr. Rimsha


 
# Magnitude Comparator

- The **comparison** of two numbers is an operation that determines if one number is **greater** than, **less** than or **equal** to the other number
- A **magnitude comparator** is a combinational circuit that compares two numbers, A and B and determines their **relative magnitudes**
- The **outcome** of the comparison is specified by **three binary variables** that indicates whether  $A > B$ ,  $A = B$  or  $A < B$



# Magnitude Comparator

- If we follow the traditional design approach of **truth table** then comparing two n-bit numbers will have  $2^{2n}$  entries in the truth table and becomes **too complicated** for large values of n.
- However, a comparator circuit possess a certain amount of **regularity**. Digital functions that possess an inherent well defined regularity can usually be designed by means of algorithmic procedure. This reduce design efforts and reduce human errors
- An **algorithm** is a procedure that specifies a finite set of **steps**, if followed, give the solution to a problem. The algorithm is direct application of the procedure a person uses to compare the relative magnitude of two numbers

# Developing Algorithm

- Consider the two numbers A and B, with four digits each, the coefficients of numbers with descending significance can be written as:
  - $A = A_3A_2A_1A_0$  and  $B = B_3B_2B_1B_0$
- The two numbers are **equal** if all **pairs** of **significant digits** are equal:
  - $A=B$  if  $A_3=B_3$ ,  $A_2=B_2$ ,  $A_1=B_1$  and  $A_0=B_0$
- For binary (either 1 or 0) digits the equality relation of each pair of bits can be expressed logically with **exclusive-NOR** function to test if  $A_i = B_i$  as
  - $x_i = (A_i \oplus B_i)' = (A_iB_i' + A_i'B_i)' = A_iB_i + A_i'B_i$  for  $i = 0, 1, 2, 3$
  - $x_i = 1$  only if the pair of bits in position  $i$  are equal otherwise  $x_i = 0$
- Therefore we can check if  $A = B$  by
  - $(A=B) = x_3x_2x_1x_0$
- The symbol  $(A=B)$  is binary output variable that is equal to 1 only if all pair of digits of the two numbers are equal

# Developing Algorithm

- To determine if  $A > B$  or  $A < B$ , we inspect the relative magnitudes of pairs of significant digits starting from the most significant position. If the two digits are equal, we compare the next lower significant pair of digits. This comparison continues until a pair of unequal digits is reached
- If the corresponding digit of A is 1 and that of B is 0, we conclude that  $A > B$ . If the corresponding digit of A is 0 and that of B is 1, we conclude that  $A < B$
- The **sequential comparison** can be expressed logically by the two Boolean functions
  - $(A > B) = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
  - $(A < B) = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$
- The symbols  $(A > B)$  and  $(A < B)$  are binary output variables that are equal to 1 when  $A > B$  or  $A < B$  respectively

# Developing Algorithm

- The gate implementation for a magnitude comparator involves a certain amount of **repetition** so it is **simpler** than it seems.
- The unequal outputs can use the same gates that are needed to generate the equal output
- The logic diagram of the 4-bit magnitude comparator is shown in fig 4 – 17
- The four x outputs are generated with exclusive-NOR circuits and applied to an AND gate to give the output binary variable (A=B)
- The other two outputs use the x variable to generate the Boolean functions
- The procedure for obtaining magnitude comparator circuits for binary numbers with more than four bits is obvious from the above steps

# 4-Bit Magnitude Comparator Logic Diagram

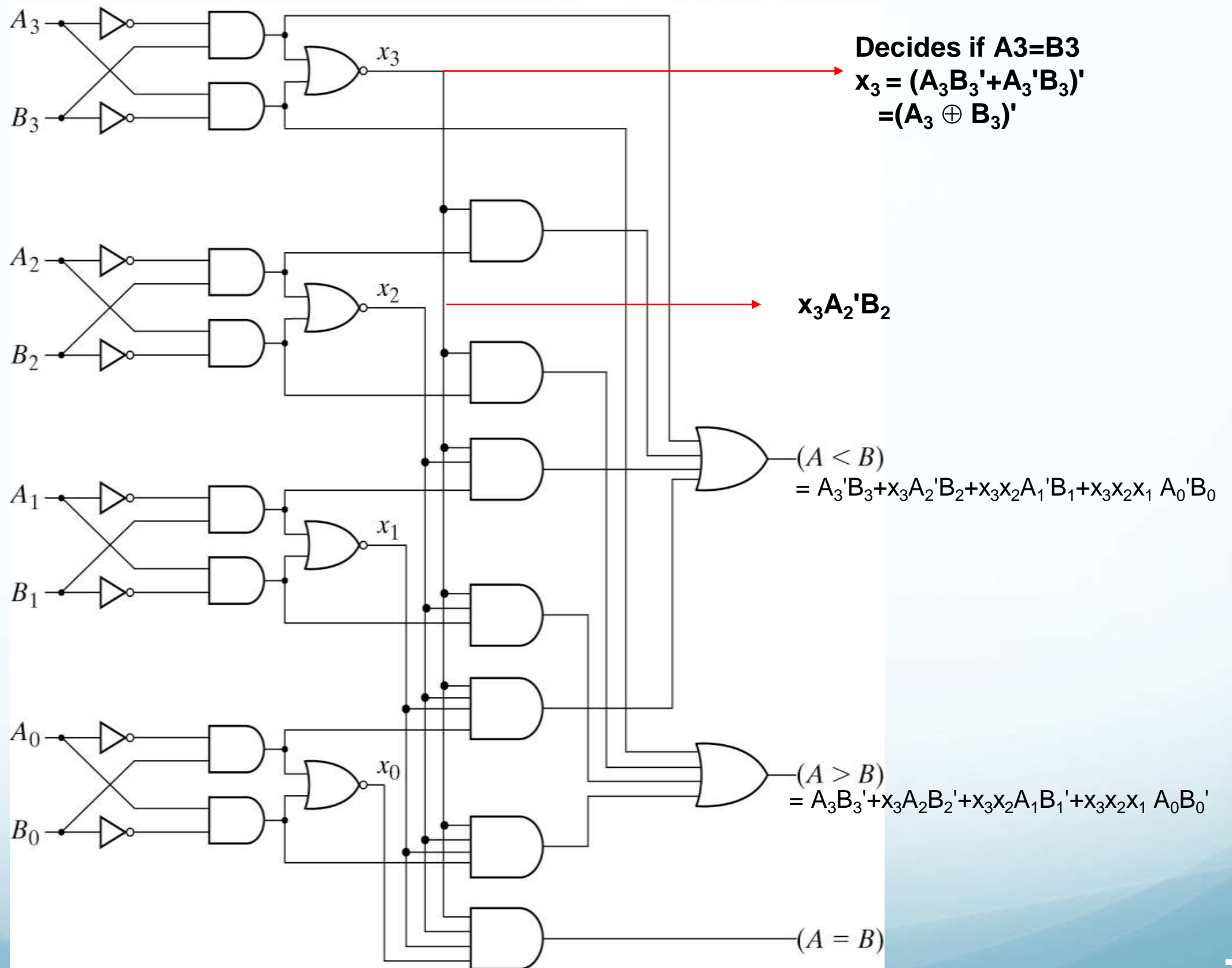


Fig. 4-17 4-Bit Magnitude Comparator




# Decoder

- What is the function of a decoder?
  - It selects or de-select one of the devices


 
# Decoder

- A decoder is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines. Only one output can be active (high) at any time
- If the  $n$ -bit coded information has unused combinations, the decoder has fewer than  $2^n$  outputs





# 3-to-8-Line Decoder

- A 3-to-8-Line Decoder is a decoder in which three inputs are decoded into eight outputs, each representing one of the minterms of the three input variables
- Each one of the eight AND gates generates one of the minterms
- A particular application of this decoder is binary-to-octal conversion, however 3-to-8-line decoder can be used for decoding any 3-bit code to provide eight outputs, one for each element of the code




# 3-to-8-Line Decoder Truth Table

Inputs			Outputs							
X	Y	Z	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1



# 3-to-8-Line Decoder Implementation

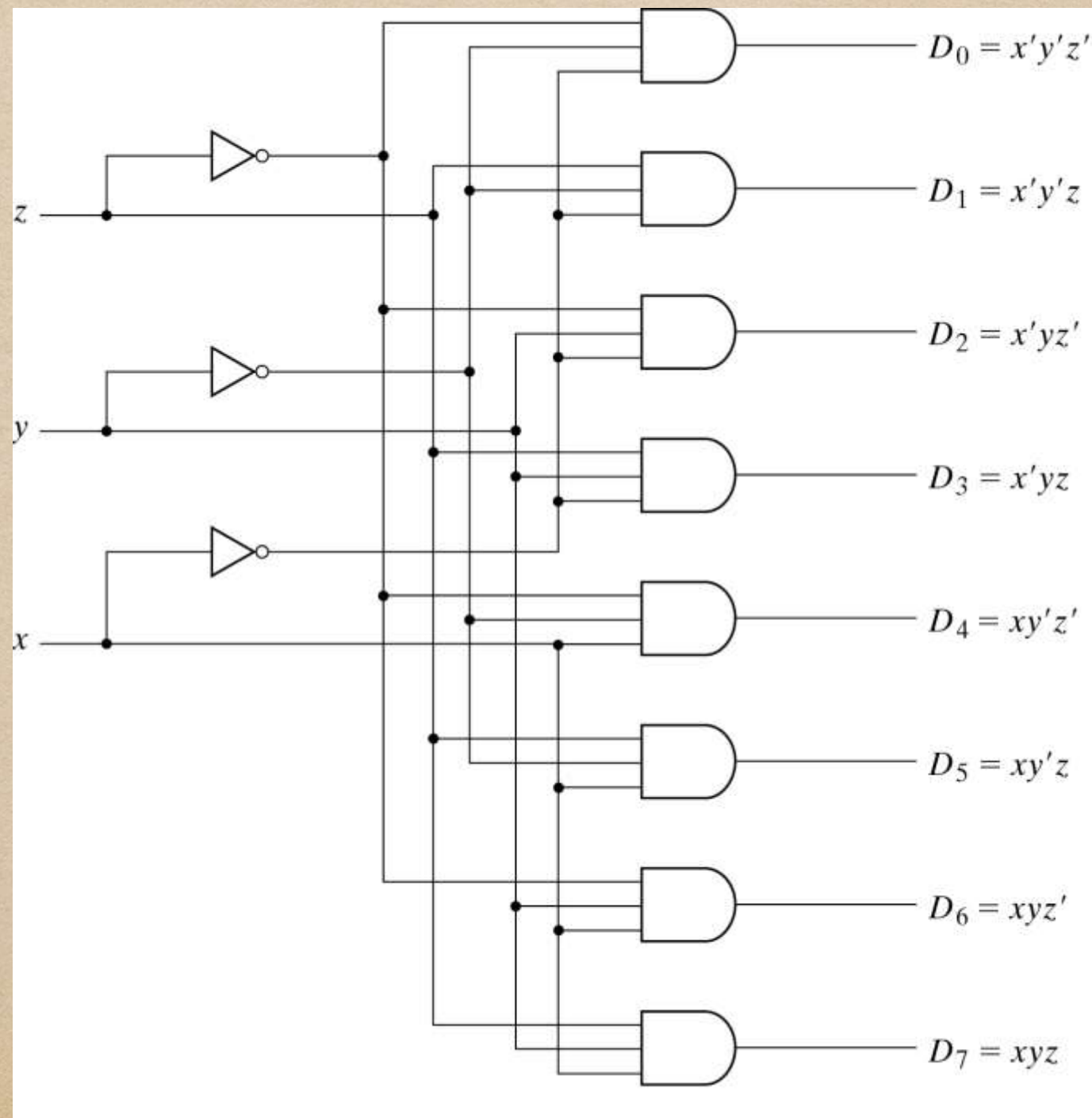




# Summary

- What is the function of a decoder?
- It selects or de-select one of the devices



# Decoders with NAND gates

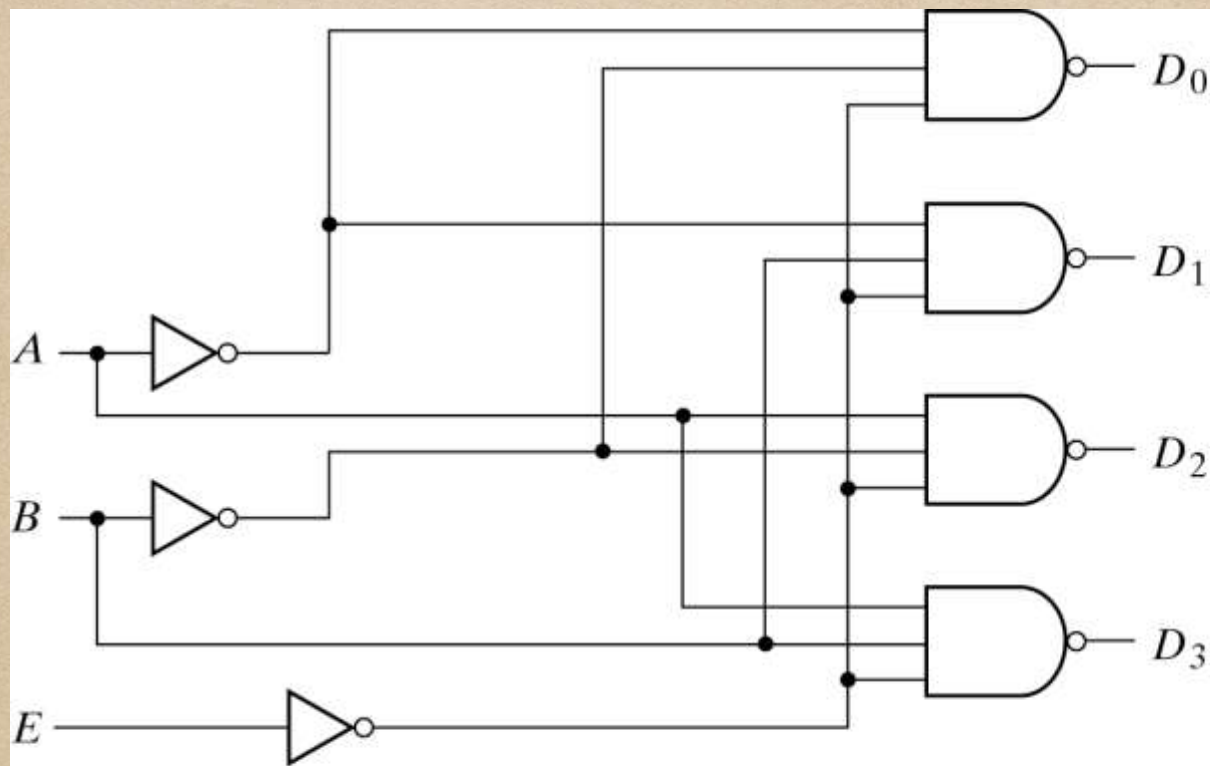

(a) Logic diagram

$E$	$A$	$B$	$D_0$	$D_1$	$D_2$	$D_3$
1	$X$	$X$	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table



End of Lecture