

# **Introduction to Sequential Logic, Latch and Flip Flop Circuits**

**By Engr. Rimsha**


- **Introduction to Sequential Logic**
  - » **Synchrononous Sequential Circuits**
  - » **Asynchronous Sequential Circuits**
- **Latches**
  - » **SR with NOR gates**
  - » **SR with NAND gates**

## Sequential Circuits

- A **sequential circuit** consists of combinational circuits to which storage elements are connected to form a feedback path.
  - **Storage elements** store binary information.
  - **Outputs** of a sequential circuit are a function of the inputs and the internal state of the storage elements.
- **State** refers to the currently known condition of the circuit including what data is stored in the storage elements.
- A **sequential circuit** is specified by a time sequence of inputs, outputs, and internal states.

## Sequential Circuit- Block Diagram

- **Block Diagram**

 

## Sequential Circuit Types


- There are two types of sequential circuits **Synchronous** and **Asynchronous** :
  - A **synchronous sequential circuit** is a system whose behavior can be defined from the knowledge of its signals at discrete instants of time
    - » Storage elements in synchronous circuits are affected at discrete instants of time
  - An **asynchronous sequential circuit** depends on the input signals at any instant of time and the order in which the inputs change
    - » Storage elements in asynchronous circuits are usually time-delay devices
    - » The storage capability of time-delay devices is due to the time it takes for the signal to propagate through the device
    - » It is also regarded as combinational circuit with feedback

## Synchronous Sequential Circuit

- Synchronization in synchronous sequential circuits is achieved by timing device called a **clock generator**
- A clock generator generate a periodic train of clock pulses
- The clock pulses are distributed throughout the system in such a way that storage elements are affected only with the arrival of each pulse
- Clock pulses are employed with other circuitry that indicates the changes to the storage elements.
- Synchronous sequential circuits that use clock pulses in the inputs of storage elements are called **clocked sequential circuits**.
- These are most commonly used having no instability problems
- The memory elements used in these circuits are **flip-flops**

# Synchronous Sequential Circuit

- **Clocked Sequential Circuit**

 

(a) Block diagram



(b) Timing diagram of clock pulses

## Flip Flop

- **The storage element used in clocked sequential circuits are called flip flops.**
  - A flip flop is a binary storage device capable of storing one bit of information.
  - It has two outputs, one for the normal value and one for the complement value
  - Multiple flip flops can be used to store multiple bits.
  - Flip flops receive their inputs from a combinational circuit and a clock signal.
  - A Flip flop maintains a binary state indefinitely until directed by an input signal to switch states. The state of a flip flop can change only during a clock pulse.



## Latches

- A flip flop circuit can maintain a binary state indefinitely until directed by an input signal to switch states.
  - Flip flops are categorized by the number of inputs they possess and the manner in which the inputs affect the binary state.
- **Latches** are the most basic flip flop and they operate with signal levels.
- Latches are the building blocks for all flip flops.

## SR Latch

- The **SR latch** is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates.
  - There are two inputs:
    - » S is for set
    - » R is for reset
  - There are two outputs Q and Q'

# Review


- Two type of Sequential Circuits?
  - Synchronous Sequential Circuits?
    - Behaviour is defined by at periodic time defined by clock
  - Asynchronous Sequential Circuits?
    - Changes can take place at any time instance
- Difference between Latch and Flip Flop?
  - Latch is level sensitive
  - Flip Flop is edge sensitive
  - Flip Flop is made up of latches

## SR Latch

- The **SR latch** is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates.
  - There are two inputs:
    - » S is for set
    - » R is for reset
  - There are two outputs Q and Q'
 
## SR Latch Logic (NOR Gates)

- The **SR** latch with **NOR** Gates has **two useful states**
  - When  $Q = 1$  and  $Q' = 0$  the latch is said to be in a set state.
  - When  $Q = 0$  and  $Q' = 1$  the latch is said to be in a reset state.
  - $Q$  and  $Q'$  are normally complement of each other. When both inputs are equal to 1 at the same time, an undefined state with both outputs equal to 0 occurs



(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0

(b) Function table


## SR Latch (NOR) Logic

- Normally the two inputs to the SR latch (NOR) are left at 0.
- If the state needs to be changed then the application of a momentary 1 to the S input causes the latch to go to the set state.
  - The S input must go back to 0 before any other changes to avoid the occurrence of the undefined state. The circuit remains in set state.
- A momentary 1 to the R input causes the latch to go to the reset state.
  - The R input must go back to 0 before any other changes to avoid the occurrence of the undefined state. The circuit remains in reset state.
- If a 1 is applied to both S and R then the outputs both go to 0, the **undefined state**.

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after S = 1, R = 0)
0	1	0	1
0	0	0	1 (after S = 0, R = 1)
1	1	0	0
 
# SR Latch Logic (NAND Gates)

- The **SR** latch with **NAND** Gates has **two useful** states
  - When  $Q = 1$  and  $Q' = 0$  the latch is said to be in a set state.
  - When  $Q = 0$  and  $Q' = 1$  the latch is said to be in a reset state.
  - $Q$  and  $Q'$  are normally complement of each other. When both inputs are equal to 0 at the same time, an undefined state with both outputs equal to 1



(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$ )
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$ )
0	0	1	1

b) Function table

# SR Latch (NAND) Logic

- Normally the two inputs to the SR latch (NAND) are left at 1.
- If the state needs to be changed then the application of a momentary 0 to the S input causes the latch to go to the set state.
  - The S input must go back to 1 before any other changes to avoid the occurrence of the undefined state. The circuit remains in set state.
- A momentary 0 to the R input causes the latch to go to the reset state.
  - The R input must go back to 1 before any other changes to avoid the occurrence of the undefined state. The circuit remains in reset state.
- If a 0 is applied to both S and R then the outputs both go to 1, the **undefined** state.

S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(after  $S = 1, R = 0$ )

(after  $S = 0, R = 1$ )



## NAND vs. NOR Implementations

- The input signals for the **NAND** latch requires the **complement** of those values used for the **NOR** latch
- Because the NAND latch requires a 0 signal it is sometimes called a  $S'-R'$  latch.

 


Fig. 5-3 SR Latch with NOR Gates


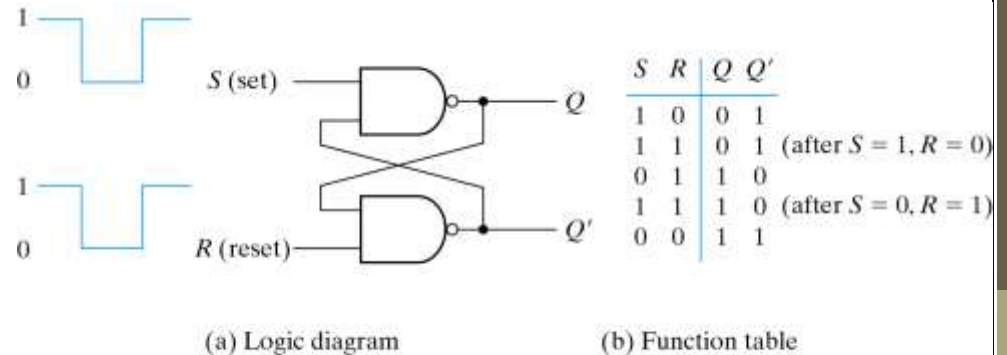


Fig. 5-4 SR Latch with NAND Gates

- D Latch Logic
- Modifying Latches to make Flip Flops

# SR Latch With Control Input

- Gated SR Latch

 

(a) Logic diagram

$C$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate


(b) Function table

## SR Latch Modification

- The basic **SR** latch can be **modified** by providing an additional **control** input that determines when the state of the latch can be changed.
  - The following example uses the C enable input with 1 allowing inputs S and R to flow through and 0 disallowing the flow of the inputs S and R. In other words S and R are allowed to change the flip-flop only when  $C = 1$  and If  $C=0$ , S and R can't change output
  - It consists of basic SR latch and two additional NAND gates
  - The control input C acts as an enable input for the other two inputs
  - The output of the NAND gates stay at the logic 1 level as long as the control input remains at 0. This is quiescent (inactive) state.
  - When the control input goes to 1, the information for S or R is allowed to effect the SR latch (active state)
  - The set state is reached with  $S=1$ ,  $R=0$  and  $C=1$ . To change to the reset state, the inputs must be  $S=0$ ,  $R=1$  and  $C=1$ . In either cases when C returns to 0, the circuit remains in its current state

# D Latch Logic

- Gated D Latch

 

(a) Logic diagram

<i>C</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state

(b) Function table

# D Latch


- A D latch modifies the SR latch to **avoid** the **undesirable condition** of the indeterminate state by ensuring that S and R are never equal to 1 at the same time.
  - There are only two inputs:
    - D is the data input
    - C is the control input
  - The D input goes directly to the S input and its complement goes to the R input.
  - When control input C is left at 0 the state of the latch remains constant (regardless of value of D).
  - If  $C = 1$  and  $D = 1$  the output Q goes to 1, placing the circuit in the set state.
  - If  $C = 1$  and  $D = 0$  the output Q goes to 0, placing the circuit in the reset state.

## Notes on D Latches


- The D Latch has the ability to **hold data** in its internal storage.
- The data **input** of the D latch is **transferred** to the Q **output** when the **control** input is **enabled**.
  - The output follows changes in the data input as long as the control input is enabled.
  - For this reason, the latch is also called the **transparent latch**.
- When the control input is disabled, the output of the latch remains in the state it was in just prior to the control input being disabled.

## Graphic Symbols for Latches


- IEEE Symbols

 

$SR$

 

$\overline{SR}$

 

$D$

**$\overline{SR}$  : NAND gate Latch**



# Problems With Latches

- The problem with the latch is that it responds to a change in the level of a clock pulse.
  - A positive level response in the control input allows changes in the output when the D input changes while the clock pulse stays at logic-1.
- The key to solving the latch problem in flip flops is to ensure that **changes** are only allowed to occur during a **signal transitions** (at the point in value change).
  - A positive transition is called a **positive-edge response**.
  - A negative transition is called a **negative-edge response**.

# Clock Responses



(a) Response to positive level



(b) Positive-edge response




(c) Negative-edge response


# Modifying Latches

- There are two ways that a **latch** can be **modified** to form a **flip-flop**.
  - One way is to employ two latches in a special configuration that isolates the output of the flip-flop from being affected while its input is changing.
  - Another way is to produce a flip-flop that triggers only during a signal transition (from 0 to 1 or from 1 to 0), and is disabled during the rest of the clock pulse duration.


# Master Slave D Flip Flop

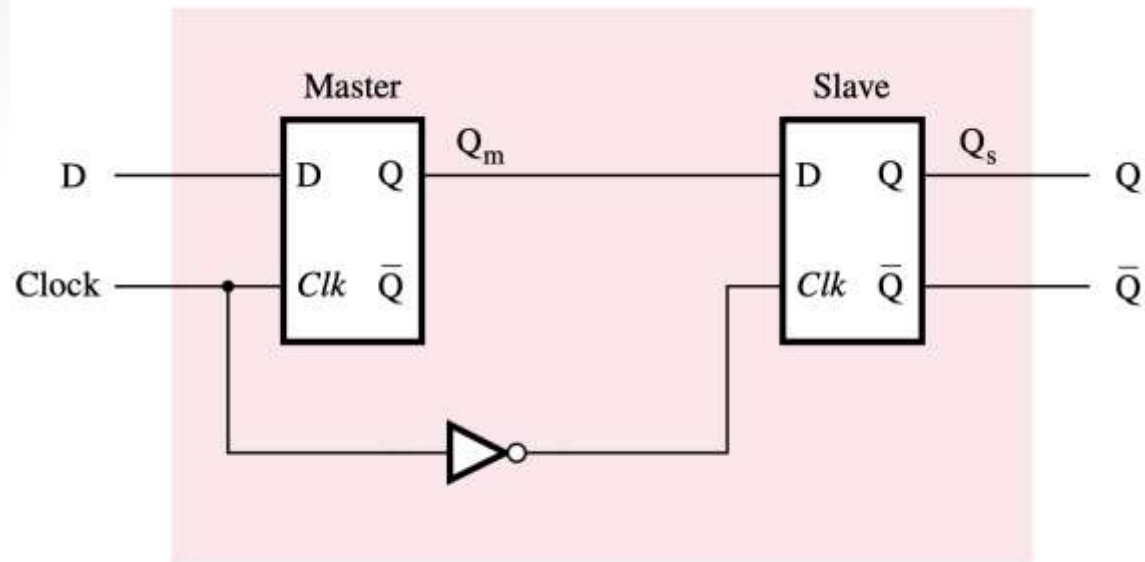

(a) Circuit

 

(b) Timing diagram

 

(c) Graphical symbol


# Edge-Triggered D Flip-Flop

- An edge-triggered D flip flop is constructed with two **D latches** and an **inverter**.
  - The first latch is called the master and second the slave.
  - The circuit samples the D input and changes its output Q only at the negative-edge of the controlling clock.
  - When the clock is 0, the output of the inverter is 1, the slave latch is enabled and its output Q is equal to the master output Y.
    - The master latch is disabled because the clock is 0.
  - When the input pulse changes to the logic 1 level, the data from the external D input is transferred to the master.
    - The slave is disabled as long as the clock remains in the 1 level because its C input is equal to 0.
    - Any change in the input changes the master output at Y, but cannot affect the slave output.
    - When the pulse returns to 0 the master is disabled and the slave is enabled causing the value of Y to be transferred to output Q.


# Edge Transition

- The previous implementation uses a negative edge transition.
  - The output only changes during the negative edge of the clock.
- A **positive edge** transition implementation can be constructed by placing an **inverter** on the CLK input prior to any other gate or inverter. i.e. between the CLK terminal and the junction between the other inverter and input C of the master latch.
- Such flip flop is triggered with a negative pulse, so that negative edge of the clock affects the master and the positive edge affects the slave and the output terminal
 
## Edge-Triggered D Flip Flop Graphic Symbols




(a) Positive-edge

 

(a) Negative-edge

# 3 – SR Latch Flip Flop

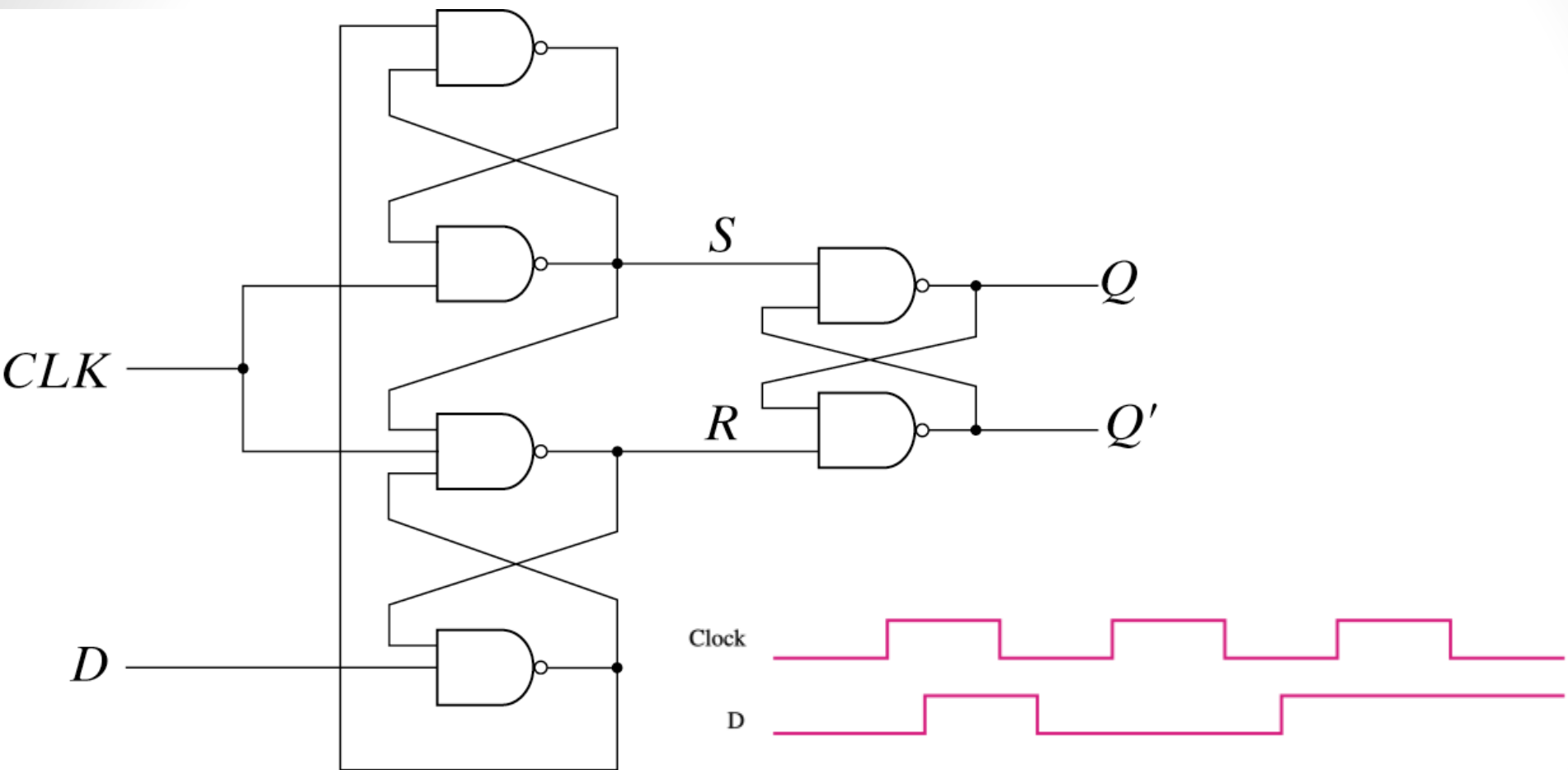



# Alternative Positive Edge Flip Flop

- A more efficient construction of an edge-triggered D flip flop uses **three SR latches**.
  - Two latches respond to the external D (data) and CLK (clock) inputs.
  - The third latch provides the outputs for the flip flop.
  - The S and R inputs of the output latch are maintained at logic 1 level when  $CLK = 0$  causing the output to remain in its present state.
  - If  $D = 0$  when  $CLK = 1$ , R changes to 0 causing a reset state and making  $Q = 0$ .
  - If there is a change in D while  $CLK = 1$ , terminal R remains at 0, thus locking out the flip flop (unresponsive to further changes in the input).
  - If  $D = 1$  when  $CLK = 1$ , S changes to 0 causing the circuit to go to the set state making  $Q = 1$ .

## D-Type Positive Edge Triggered Flip Flop – Summary

- When the input clock makes the positive transition, the value of D is transferred to Q
- A negative transition from 1 to 0 (or steady CLK state: logic 1 or logic 0 ) doesn't affect the output
- This flip flop respond to transition from 0 to 1 only

# Notes on Flip Flops

- The timing of the response of a flip flop to input data and clock must be taken into consideration when using edge-triggered flip flops.
- There is a minimum time, called **setup time**, for which the D input must be **maintained** at a constant value prior to the occurrence of the clock transition.
- There is a minimum time, called **hold time**, for which the D input must **not change** after the application of the positive transition of the clock.
- The **propagation delay time** of the flip flop is defined as the time interval between the trigger edge and the stabilization of the output to a new state.

The End