

## **Analysis and Design of Combinational Circuit, Half Adder, Full Adder, Adder/Subtractor**

**Instructor: Engr. Rimsha**


# Prime Implicants

$$F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

**Prime implicant** is a product term obtained by combining the maximum possible number of adjacent squares in the map


If a minterm in a square is covered by only one prime implicant, that prime implicant is said to be **Essential Prime Implicant**

# Essential Prime Implicant

 

Note:  $A'B'C'D' + A'B'CD' = A'B'D'$   
 $AB'C'D' + AB'CD' = AB'D'$   
 $A'B'D' + AB'D' = B'D'$

 (a) Essential prime implicants  
 $BD$  and  $B'D'$



(b) Prime implicants  $CD$ ,  $B'C$ ,  
 $AD$ , and  $AB'$

$$\begin{aligned} F &= BD + B'D' + CD + AD \\ &= BD + B'D' + CD + AB' \\ &= BD + B'D' + B'C + AD \\ &= BD + B'D' + B'C + AB' \end{aligned}$$

# Essential Prime Implicant Example

$$G(W,X,Y,Z) = \Sigma m(0, 1, 3, 7, 8, 11, 12, 13, 15)$$

$$F = YZ + W'X'Y' + X'Y'Z' + WXY'$$

$$F = YZ + W'X'Y' + WY'Z' + WXY'$$


$$F = YZ + W'X'Y' + WY'Z' + WXZ$$

# Essential Prime Implicant

✓  
 $F_1 z = yz + x'y'z + w'x'y + wxz$
 
## Example

$$G(W,X,Y,Z) = \sum m(0, 1, 3, 7, 8, 11, 12, 13, 15)$$



Essential =  $yz$  (3, 7, 11, 15)

PIs =  $x'y'z$ ,  $w'x'y$ ,  $w'y'z$ ,  $wx'y$ ,  $wxz$


Patrick Method.

Prime Impl	Comb	0	1	8	12	13
* $yz$	(3, 7, 11, 15)			x		
A $x'y'z$	(0, 8)	x				
B $w'x'y$	(0, 1)	x	x			
C $w'x'z$	(1, 3)		x			
D $w'y'z$	(8, 12)			x	x	
E $wx'y$	(12, 13)				x	x
F $wxz$	(13, 15)					x

✓  
 $G = (A+B)(B+C)(A+D)$   
 $= (A+BD)(B+C)(D+E)(E+F)$   
 $= [AB + AC + BD + BCD][E+DF]$   
 $= ABE + ACE + BDE + BCD + ADF + ACD + BDF + BCD$
 
# Essential Prime Implicant Example Solution

$$G(W,X,Y,Z) = \sum m(0, 1, 3, 7, 8, 11, 12, 13, 15)$$



EPI  
PI  
0, 1, 8, 12, 13

$yz$   
 $x'y'z'$ ,  $w'x'y'$ ,  $w'y'z'$ ,  $w'x'z$   
 $m_0, m_8$ ,  $m_1, m_3$ ,  $m_4, m_{12}$ ,  $m_{13}, m_{15}$   
 $wxz$   
 $wx'y'$

①  $F = yz + x'y'z' + w'x'z + wx'y'$

✓ ②  $F = yz + x'y'z' + w'x'y' + wxz$



✓ ③  $F = yz + w'x'y' + w'y'z' + wxz$

✓ ④  $F = yz + w'x'y' + w'y'z' + wx'y'$


  
# Combinational Circuits

- \* Logic circuits for digital system may be **combinational** or **sequential**
  - \* A **combinational** circuit consists of logic gates whose outputs are a function of the **current inputs**
  - \* **Sequential circuits**
    - \* contains **storage elements** in addition to logic gates
    - \* the outputs are a function of the current inputs and the state of the memory (storage) elements
    - \* The state of storage elements, in turn, is a function of previous inputs so outputs also depend on **past inputs**
    - \* They have **feedback** connection



# Analysis Procedure


- \* The analysis of a combinational circuit requires that we determine function that the circuit implements
- \* The first step in analysis procedure is to make sure that the given circuit is **combinational** and **not sequential** (No feedback path)
- \* To obtain the output Boolean function from a logic diagram we proceed as follows
  - \* Label all gate outputs that are a function of input variables with arbitrary symbols. Determine the Boolean function for each gate output
  - \* Label the gates that are a function of input variables and previously labeled gates with other arbitrary symbols. Find the Boolean function of these gates
  - \* Repeat the above process (step 2) until the outputs of the circuit are obtained
  - \* By repeated substitution of previously defined functions, obtain the output Boolean functions in terms of input variables



# Combinational Circuits

- \* For  $n$  input variables there are  $2^n$  possible binary input combinations
- \* For each possible input combination there is one possible output value
- \* The most important standard combinational circuits (discussed in this chapter) are **adders**, **subtractors**, **comparators**, **decoders**, **encoders**, and **multiplexers**
- \* If the storage registers are included with the combinational gates then this circuit is considered as sequential circuit

# Analysis Procedure-Example

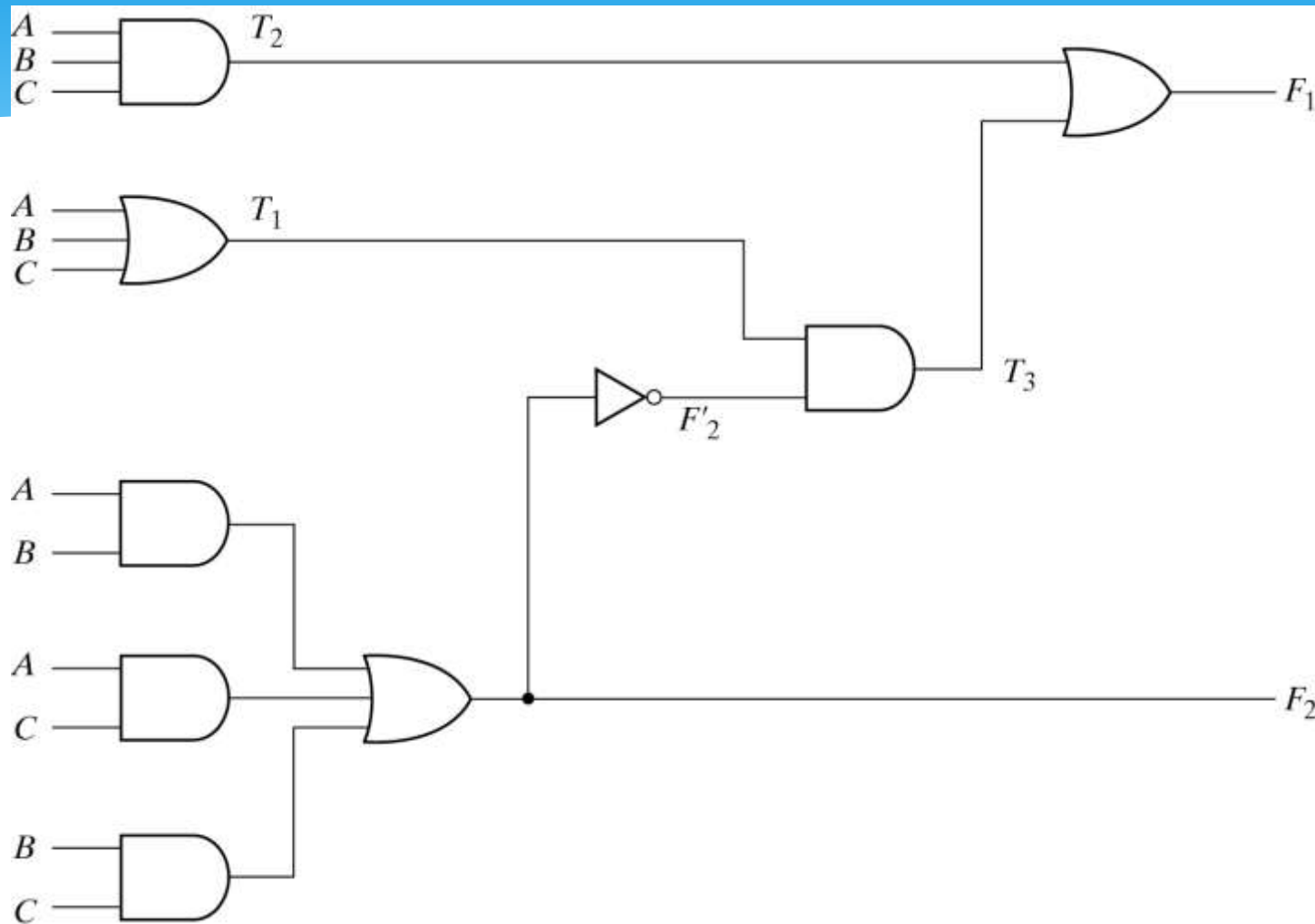

# Analysis Procedure-Example

- \* The circuit has three binary inputs- A, B and C and two binary outputs-  $F_1$  and  $F_2$
- \* The outputs of various gates are labeled with intermediate symbols
- \* The output of gates that are a function of input variables are  $T_1$  and  $T_2$
- \* Output  $F_2$  can be easily derived from the input variables
- \* The Boolean function for these three outputs are:
  - \*  $F_2 = AB + AC + BC$
  - \*  $T_1 = A + B + C$
  - \*  $T_2 = ABC$
- \* Next we consider output of gates that are a function of already defined symbols
  - \*  $T_3 = F_2' T_1$
  - \*  $F_1 = T_3 + T_2$

# Analysis Procedure-Example

- \* To obtain  $F_1$  as a function of A,B and C, from a series of substitutions proceed as follows

$$\begin{aligned}F_1 &= T_3 + T_2 \\&= F_2' T_1 + ABC \\&= (AB + AC + BC)'(A + B + C) + ABC \\&= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\&= (A' + B'C')(AB' + AC' + BC' + B'C) + ABC \\&= A'BC' + A'B'C + AB'C' + ABC \\F_2 &= AB + AC + BC\end{aligned}$$

- \* These functions  $F_1$  and  $F_2$  implement circuit of a **full-adder**.  
Where:

- \*  $F_1$  is the sum
- \*  $F_2$  is the carry

# Derivation of the Truth Table

- \* The derivation of the truth table for the circuit is a straight forward process once the output Boolean functions are known
- \* To obtain the **truth table** directly from the **logic diagram** without going through the derivations of the Boolean functions, we proceed as follows:
  - \* Determine the number of input variables in the circuit. For  $n$  inputs, form the  $2^n$  possible input combinations and list binary numbers from 0 to  $2^n - 1$  in a table
  - \* Label the outputs of selected gates with arbitrary symbols
  - \* Obtain the truth table for the outputs of those gates that are a function of the input variables only
  - \* Proceed to obtain the truth table for the outputs of those gates that are function of previously defined values until the columns for all outputs are determined

# Truth Table for Fig 4-2

- \*  $F_2$  equal to 1 for any combination that has 2 or 3 inputs equal to 1
- \*  $F_2'$  is the complement of  $F_2$
- \*  $T_1$  and  $T_2$  are the OR and AND functions of input variables respectively
- \*  $T_3 = 1$ , when  $T_1$  and  $F_2'$  are equal to 1
- \*  $F_1 = 1$ , when either  $T_2$  or  $T_3$  or both are equal to 1

$A$	$B$	$C$	$F_2$	$F_2'$	$T_1$	$T_2$	$T_3$	$F_1$
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1



# Design Procedure

- \* The **design procedure** of combinational circuits involves following steps
  - \* State the problem (Circuit specifications)
  - \* From the circuit specifications determine the inputs and outputs
  - \* The input and output variables are assigned symbols
  - \* Derive the truth table that gives the relationship between inputs and outputs
  - \* Derive the simplified Boolean functions (simplify by algebraic manipulation or K-map method) for each output as a function of input variables
  - \* Draw the logic diagram and verify the correctness of the design

# Practical Design Considerations

- \* Logic **minimization** must consider practical design constraints such as:
  - \* number of gates
  - \* number of inputs to a gate
  - \* propagation delay of signal through the gates
  - \* number of interconnection
  - \* limitations of the driving capabilities of each gate
- \* In most cases the simplification begins by satisfying an elementary objective – producing the simplified Boolean function in a standard form, and the proceed with further steps to meet other performance criteria

# Code conversion example

- \* Different digital systems use different types of **codes**
- \* It is sometimes necessary to use the output of one system as the input to another
- \* A **conversion circuit** must be inserted between the two systems if each uses different codes for the same information
- \* A code converter is a circuit that makes the two systems **compatible** even though each uses a **different binary code**
- \* To convert from binary code A to binary code B, the **input** lines (of combinational circuit) must supply the bit combination of elements as specified by **code A** and the **output** lines must generate the corresponding bit combination of **code B**

# Code conversion: BCD to Excess-3 Code

- \* Each code uses four bits to represent a decimal digit, there must be four input variables and four output variables
- \* Designate the four input binary variables by the symbols A,B,C,D and the four output variables by w, x, y and z.
- \* The truth table relating the input and output variable is made (shown in next slide)
- \* Four binary variables have 16 bit combinations but only 10 are listed in the truth table as 6 bit combinations not listed are don't care conditions. These have no meaning in BCD

# Code conversion: Truth Table





Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

# K-Maps

- \* There are four outputs, each as a function of four input variables.
- \* There are four maps, each representing one of the outputs, to obtain simplified Boolean functions.
- \* The 1's marked inside the squares are obtained from the minterms that make the output equal to 1
- \* The 1's are obtained from the truth table by going over the output columns one at a time.
- \* The 6 don't care minterms 10 through 15 are marked with an X



# The Maps

    

# BCD to Excess-3 Code Converter

- \* The simplified functions

- \*  $z = D'$

- \*  $y = CD + C'D'$

- \*  $x = B'C + B'D + BC'D'$

- \*  $w = A + BC + BD$

- \* A two-level logic diagram may be obtained directly from the above Boolean expressions but there are various other possibilities for logic diagram that implements this circuit

- \* Another implementation

- \*  $z = D'$

- \*  $y = CD + C'D' = CD + (C+D)'$


- \*  $x = B'C + B'D + BC'D' = B'(C+D) + B(C+D)'$

- \*  $w = A + BC + BD$

# BCD-to-Excess Code Converter: continued

- \* The purpose this **manipulation** is to use common gates for two or more outputs
- \* This is implemented with three levels of gates
- \* OR gate with output  $C+D$  is used to implement partially each of three outputs
- \* Implementation with original sum of products require seven AND gates and three OR gates whereas after manipulation we require four AND gates and four OR gates
- \* In this way the logical circuit has been implemented in a much **economical way**.
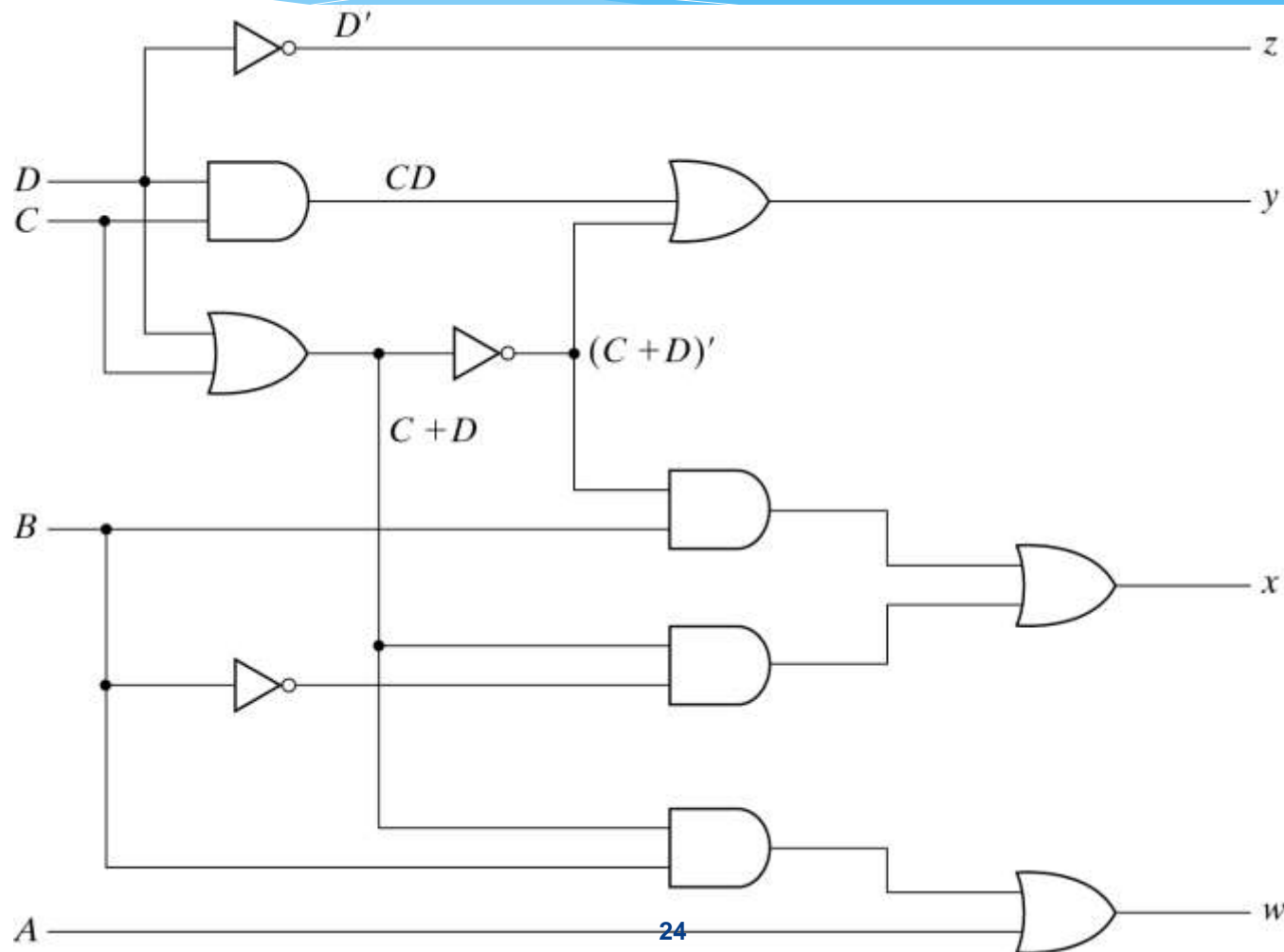
# Logic Diagram : BCD-to-Excess Code Converter





The End