


Other Flip Flops, Analysis of Sequential Circuits

By Engr. Rimsha


JK Flip Flop

- The **JK flip flop** performs three operations:
 - set it to 1
 - reset it to 0
 - complement the output
- The **J** input **sets** the flip flop to 1.
- The **K** input **resets** the flip flop to 0.
- When both J and K are **enabled**, the output is **complemented**.

JK Flip Flop Logic

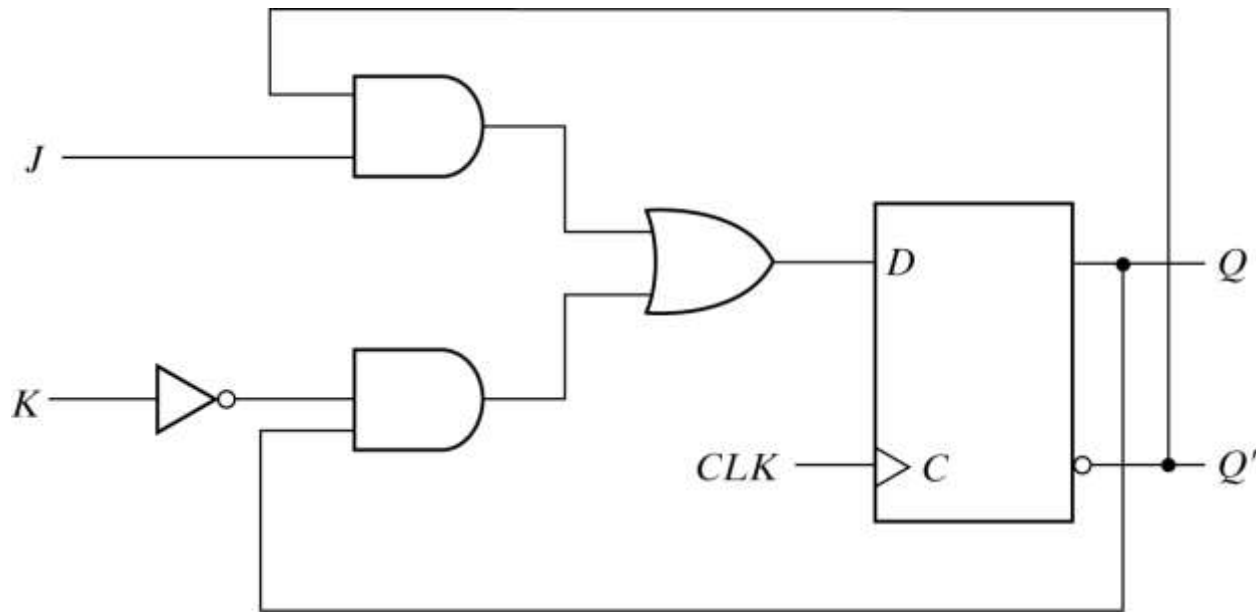

(a) Circuit diagram

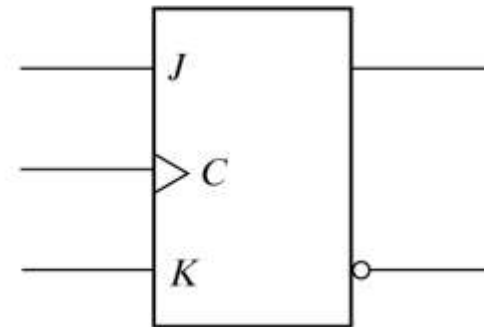

(b) Graphic symbol

Analysis of the JK Circuit

- The circuit applied to the D input is

$$D = JQ' + K'Q$$

- If $J = 1$ and $K = 0$, $D = Q + Q' = 1$, set to 1
- If $J = 0$ and $K = 1$, $D = 0$, reset to 0
- If $J = K = 1$, $D = Q'$, complements the output
- If $J = K = 0$, $D = Q$, leaving the output unchanged

JK Characteristic Table


JK Flip Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

$$Q(t+1) = J(t)Q'(t) + K'(t)Q(t)$$

T Flip Flop

- The **T (Toggle)** flip flop is a **complementing** flip flop and can be obtained from a JK flip flop when inputs J and K are **tied** together.
- The T flip flop can be obtained from a D flip flop by using an **XOR** as the **input** for D.
 - The expression for D input is $D = T \oplus Q = TQ' + T'Q$
 - When $T = 0$, ($j = k = 0$) then $D = Q$ and there is no change in the output
 - When $T = 1$, ($j = k = 1$) then $D = Q'$ and the output complements

T Flip Flop Logic

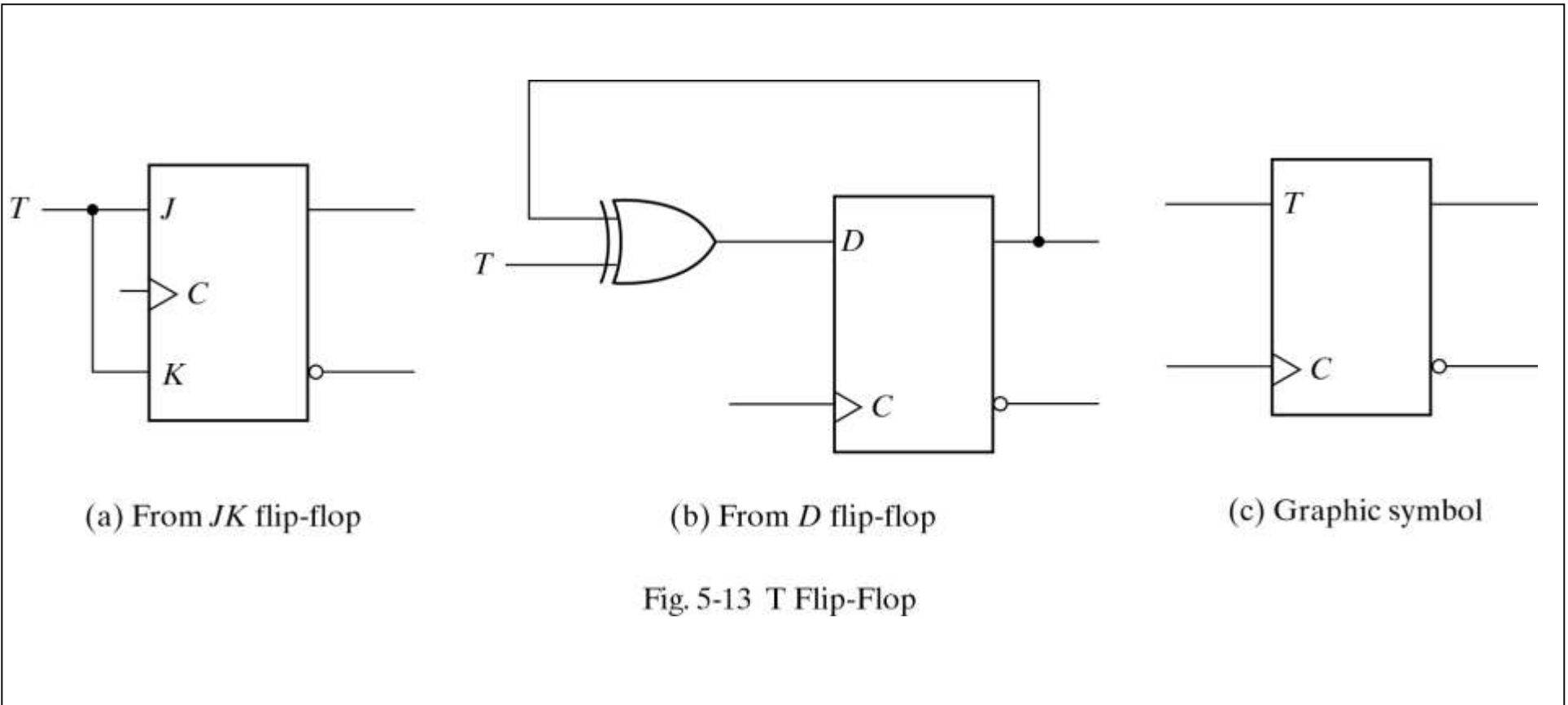

Characteristic Tables

- **Characteristic tables** define the logical properties of a flip flop by describing its operations in tabular form.
 - They define the next state as a function of the inputs and the present state.
 - $Q(t)$ refers to the present state prior to the application of a clock edge.
 - $Q(t + 1)$ refers to the next state one clock period later.
 - Clock edges are not listed as inputs but are implied by the transition from t to $t + 1$.

T Flip Flop Characteristic Table



T Flip Flop		
T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

$$Q(t + 1) = TQ' + T'Q$$



Characteristic Equations

- The **D** flip flop can be expressed as:
 - $Q(t + 1) = D$
- The **JK** flip flop can be expressed as:
 - $Q(t + 1) = JQ' + K'Q$
- The **T** flip flop can be expressed as:
 - $Q(t + 1) = TQ' + T'Q$

Direct Input to Flip Flops

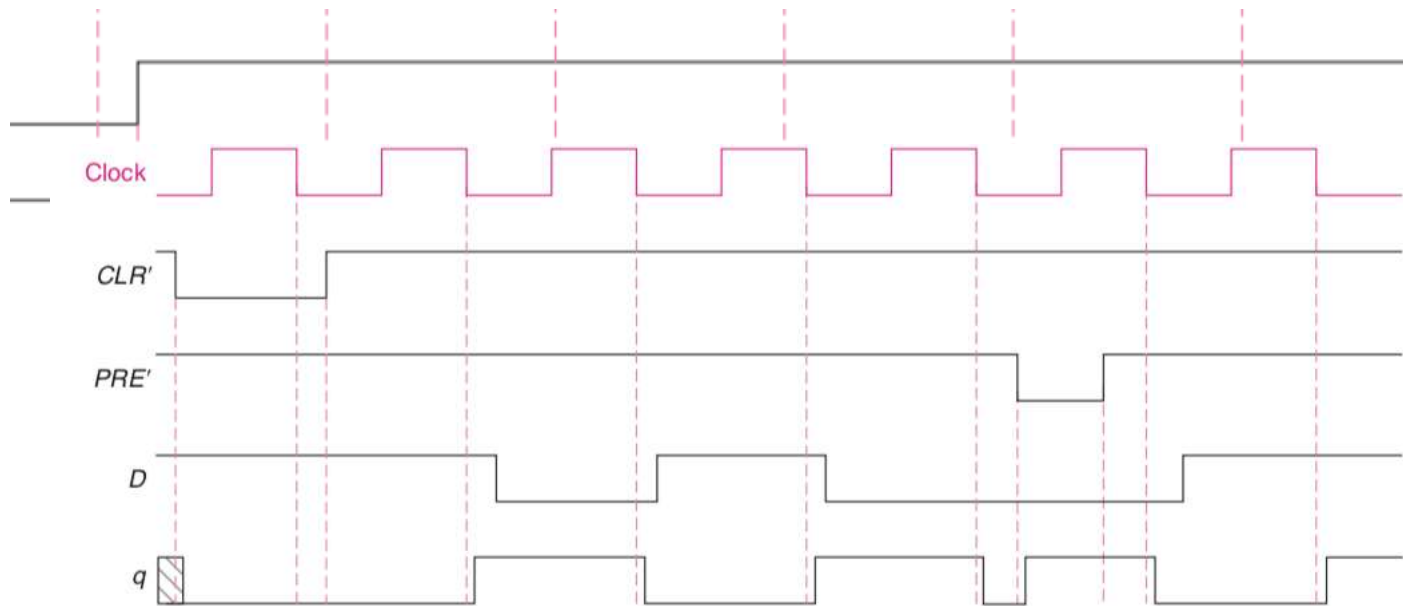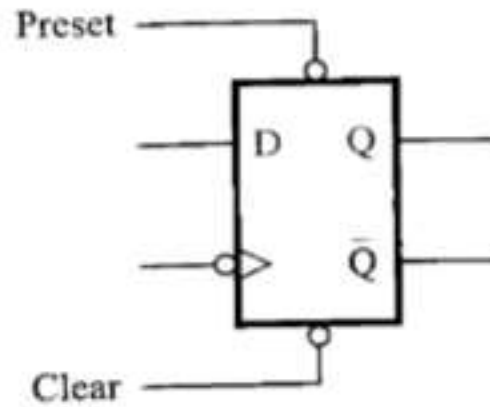


D Flip Flop with Asynchronous Reset

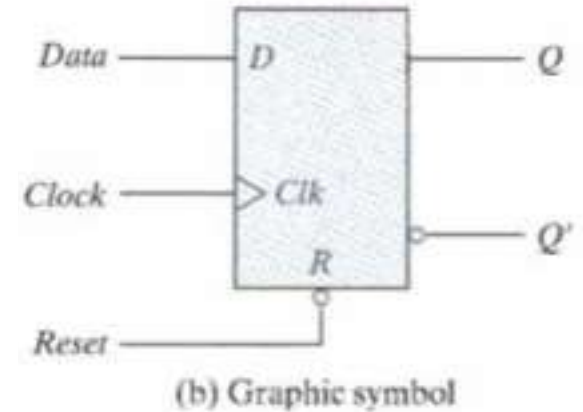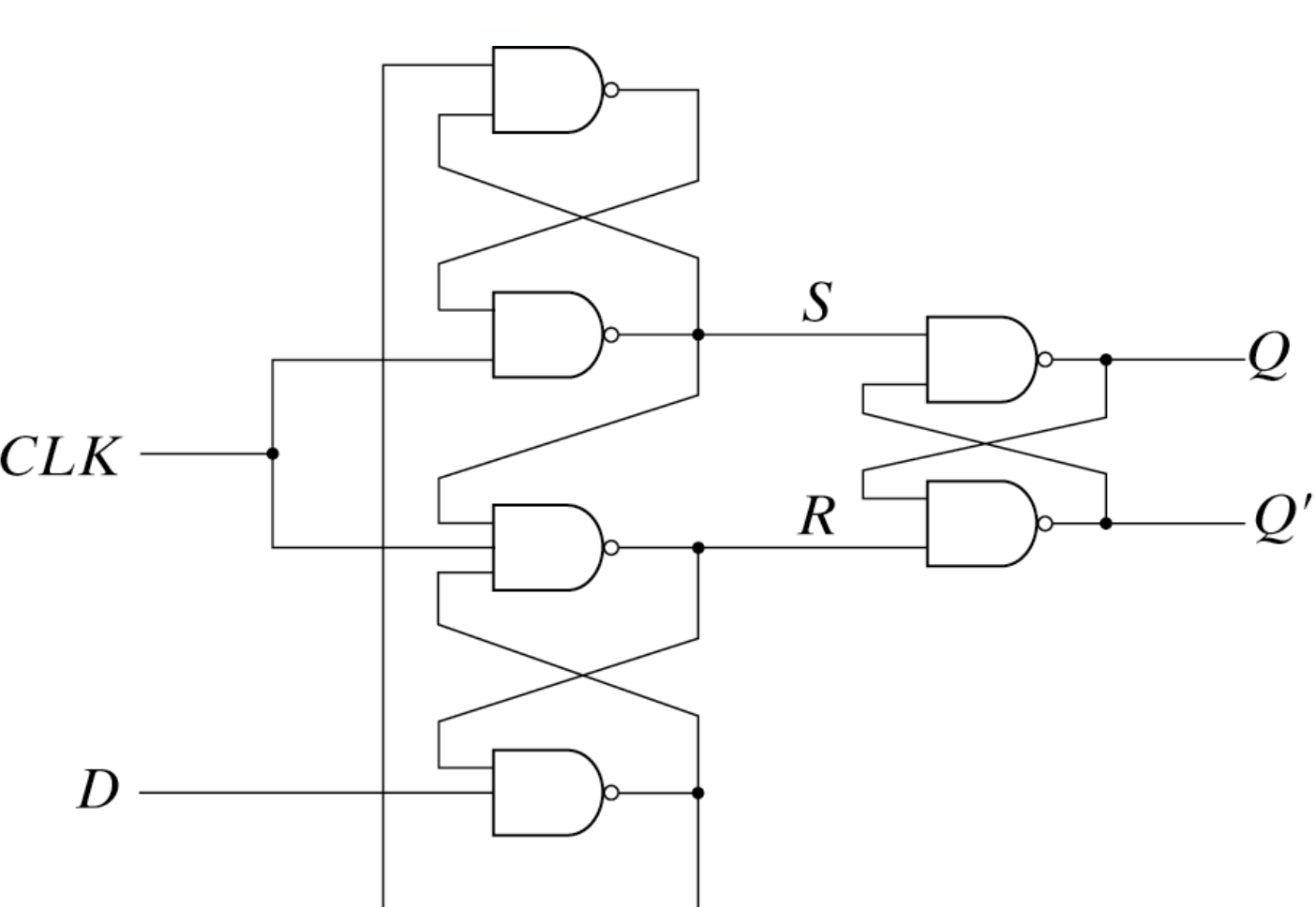

R	Clk	D	Q	Q'
0	X	X	0	1
0	↑	0	0	1
0	↑	1	1	0

(b) Function table


Solution

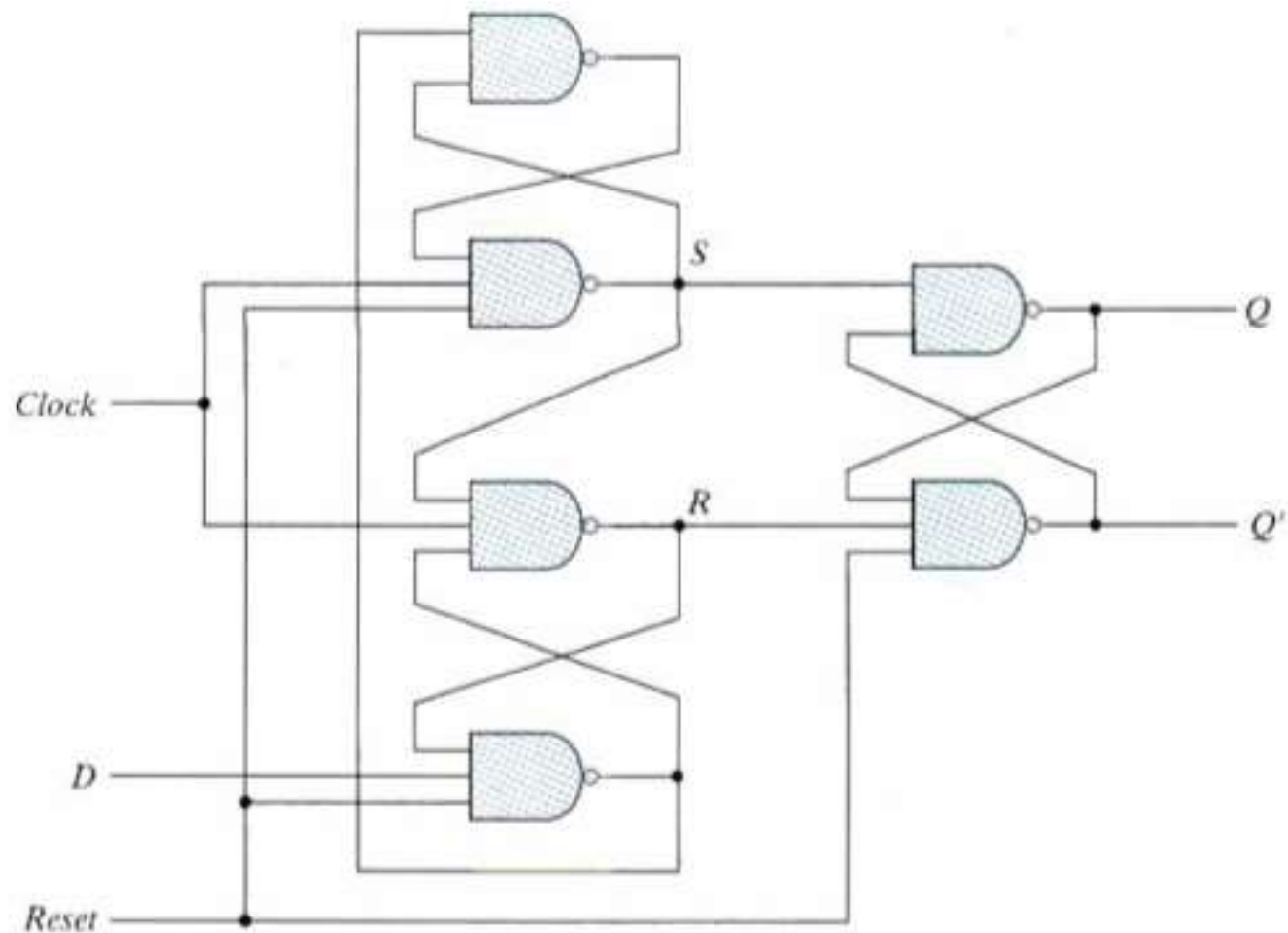

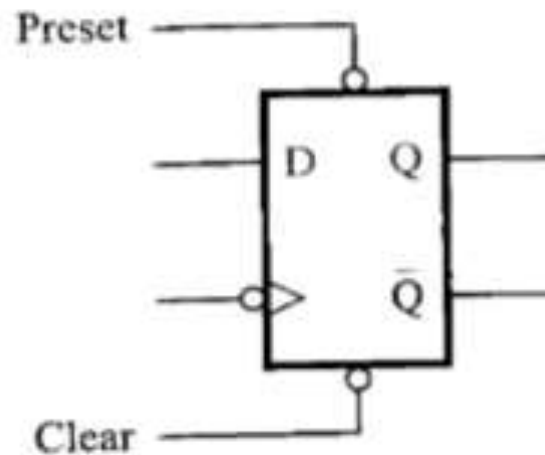(a) Circuit diagram


Practice Problem

- Make changes in circuits of Master-Slave D Flip Flop with NAND Gates into D flip flop with Clear and Preset inputs





Solution

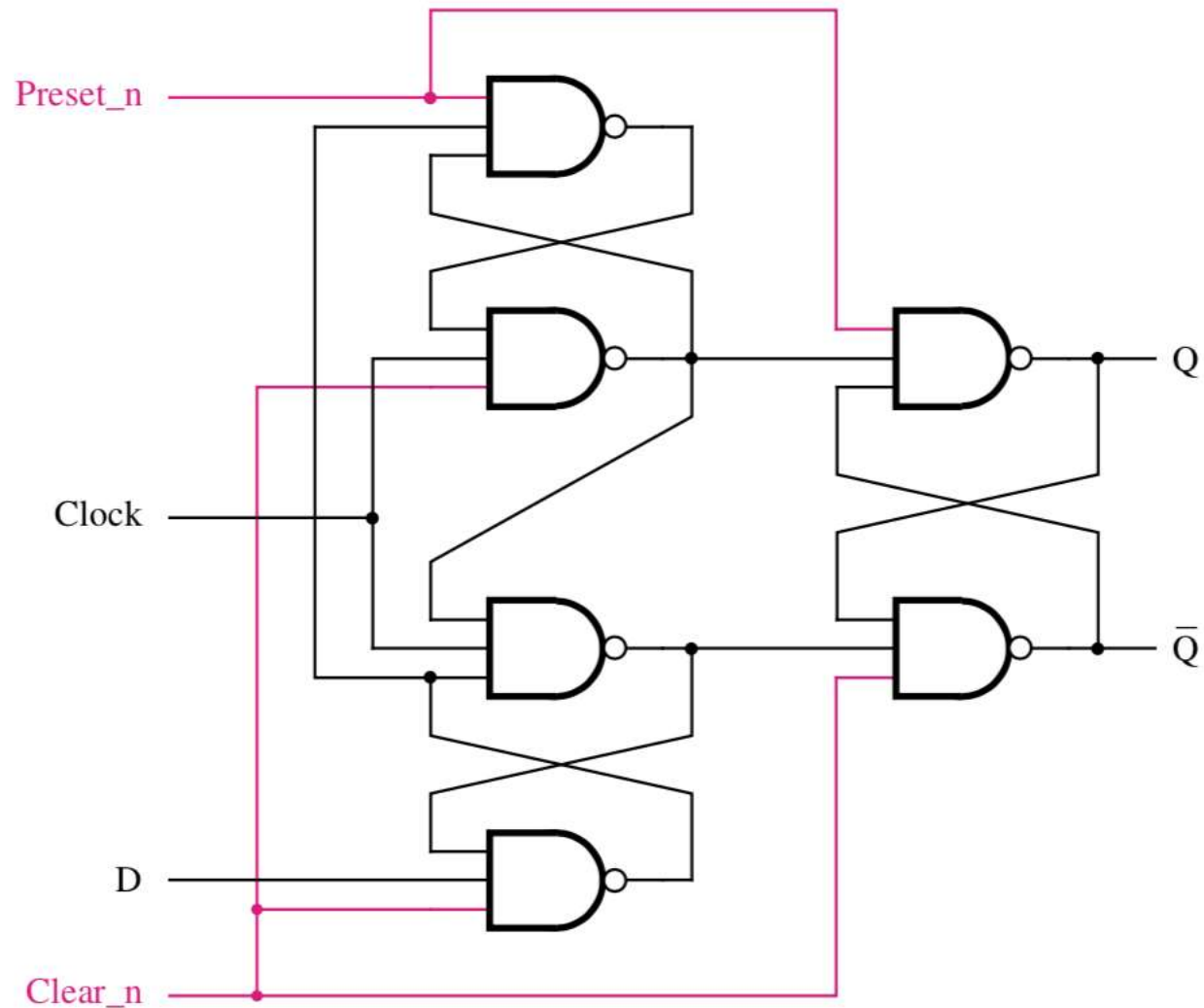Positive-edge-triggered D flip-flop with *Clear* and *Preset*



Asynchronous Vs Synchronous Reset

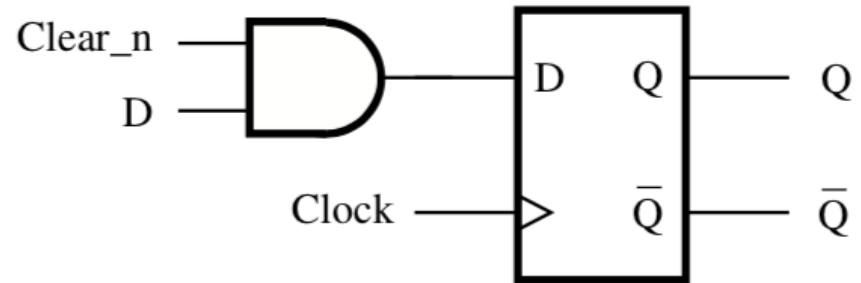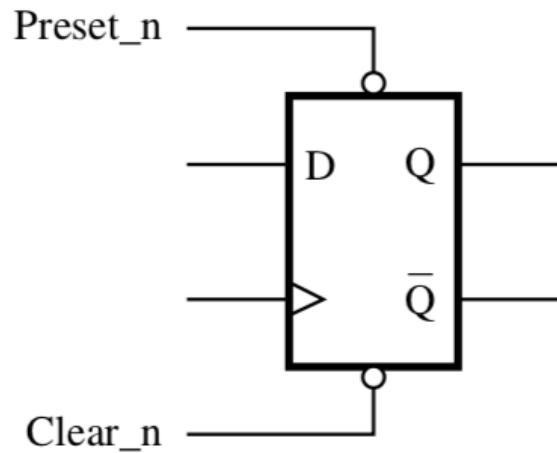

Overview

– D Flip Flop

- Characteristic Table?
- Characteristic Equation?

– JK Flip Flop


- Characteristic Table?
- Characteristic Equation?

– T Flip Flop

- Characteristic Table?
- Characteristic Equation?

- Analysis of Clocked Sequential Circuits
 - Circuit with D flip flops
 - Circuit with T or JK flop flops

Example Sequential Circuit

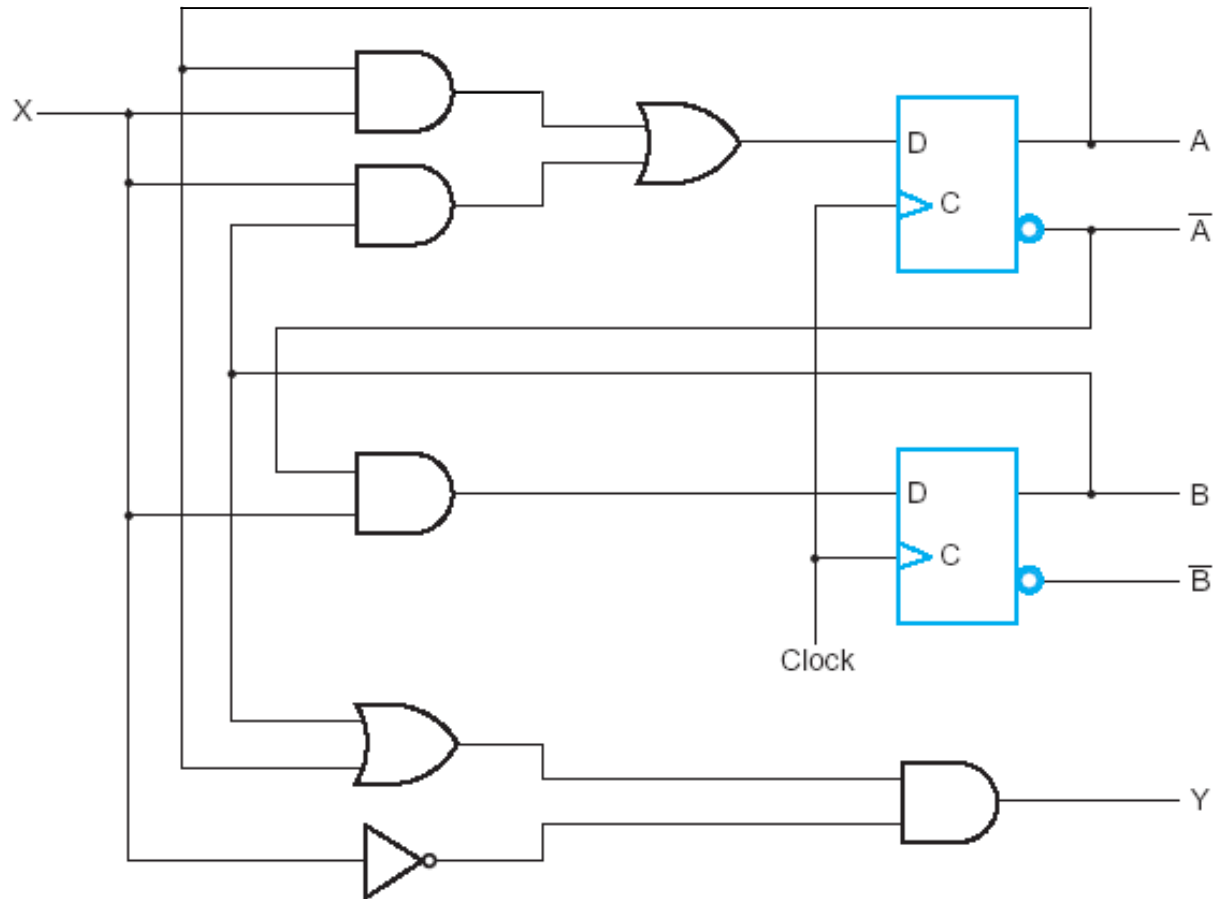


Analysis of Clocked Sequential Circuits

- The behavior of a clocked sequential circuit is determined from the inputs, the outputs, and the state of its flip flops.
 - The outputs and the next state are both a function of the inputs and the present state.
- Analysis consists of obtaining a table or a diagram for the time sequence of inputs, outputs, and internal states.
- It is also possible to write Boolean expressions that describe the behavior.

State Equations

- A **state equation** (**transition equation**) specifies the next state as a function of the present state and inputs.
 - It is an algebraic equation that specifies the condition for a flip flop state transition.

State Equations

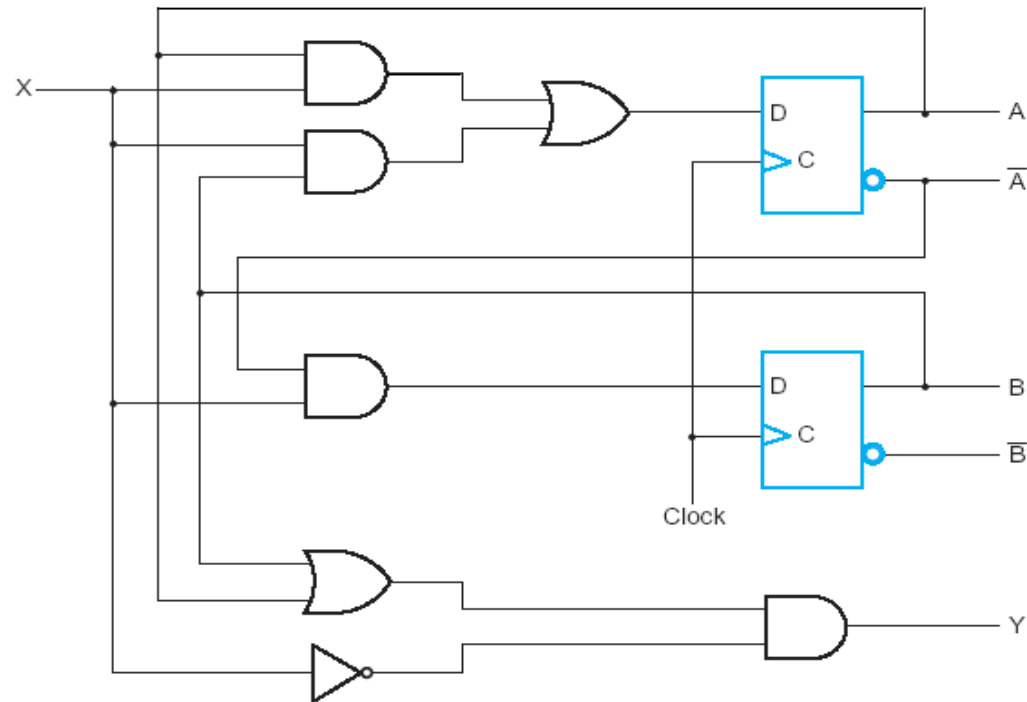

- **Since the D input determines the next state:**
 - $A(t + 1) = A(t)x(t) + B(t)x(t) = Ax + Bx$
 - $B(t + 1) = A'(t)x(t) = A'x$
 - $y(t) = [A(t) + B(t)]x'(t) = (A + B)x'$

State Table

- The time sequence of inputs, outputs, and flip flop states can be enumerated in a state table (transition table).
 - The table consists of four sections
 - **Present** state shows the states of the flip flops at time t
 - **Input** gives input values for each possible present state
 - **Next state** shows the states of the flip flops one cycle later at $t + 1$
 - **Output** gives the value of other outputs at time t for each present state and input condition

Our Example

- The derivation of a state table requires listing all possible binary combinations of present state and inputs.
 - In our example, we have eight combinations from 000 to 111.
- The next state values are then determined from the logic diagram or from the state equations.

Example State Table

- $A(t + 1) = Ax + Bx$
- $B(t + 1) = A'x$
- $y(t) = (A + B)x'$

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Generic Procedure

- A sequential circuit with m flip flops and n inputs needs 2^{m+n} rows in the state table.
- The numbers 0 through $2^{m+n} - 1$ are listed under the present state and input columns.
- The next state section has m columns, one for each flip flop.
 - Next state values are derived from the state equations.
- The output section has many columns as there are output values
 - Output values are derived from the circuit or the Boolean function in the same matter as a truth table.

Alternative Table

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


Present State		Next State			Output	
		x = 0	x = 1		x = 0	x = 1
AB		AB	AB			y
00		00	01		0	0
01		00	11		1	0
10		00	10		1	0
11		00	10		1	0

State Diagram


- Information in a state table can be represented graphically in the form of a state diagram.
- In a state diagram:
 - a state is represented by a circle
 - transitions between states are indicated by directed lines connecting the circles
 - Binary numbers inside the circles represent state of the flip flops
 - Directed lines are labeled with two binary numbers separated by a slash
 - The input value during the present state is labeled first
 - The second number gives the output after the present state with the given input

Example State Diagram

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
AB	AB	AB	y	
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

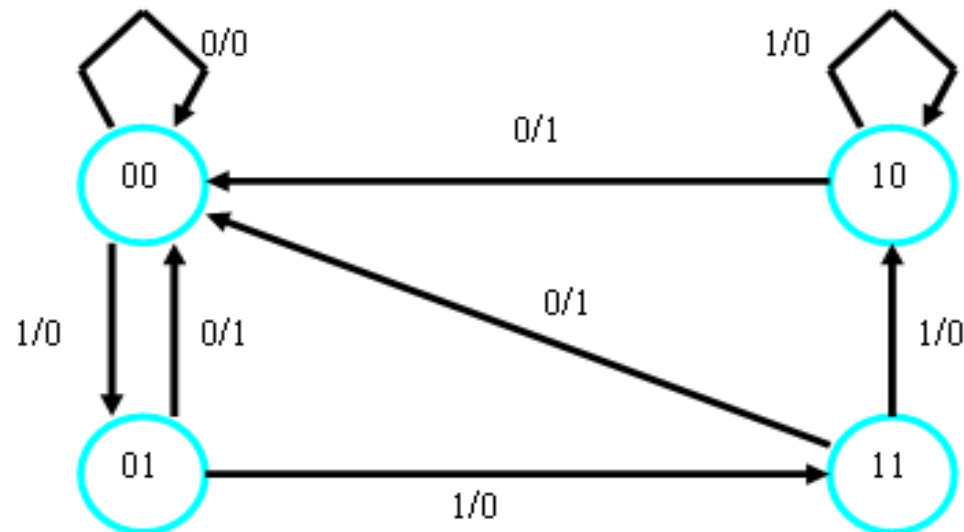


Example Analysis

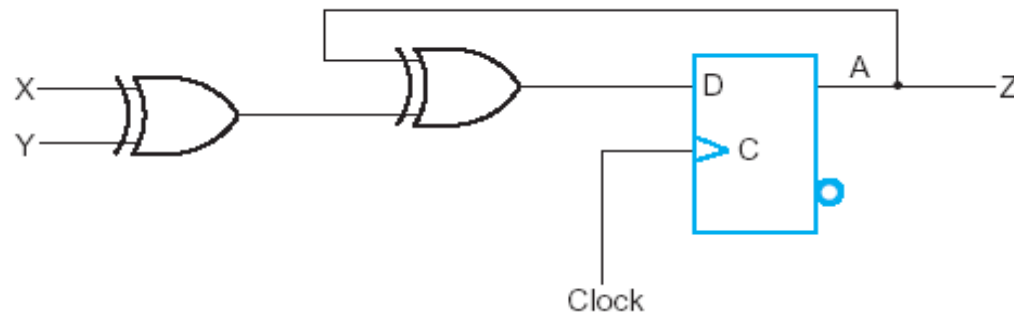

Present state	Inputs		Next state
A	X	Y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

❖ $D_A = A \oplus x \oplus y$

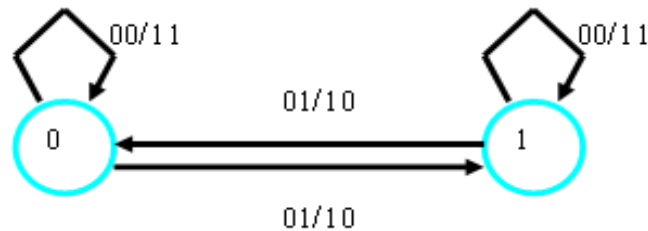

End of Lecture