



Half Adder, Full Adder, Adder/Subtractor

Instructor Name: Engr. Rimsha

Design Examples

- Binary Adder-Subtractor
 - Half Adder
 - Full Adder
- Carry Lookahead Generator

Binary Adder-Subtractor

- Digital computers perform various arithmetic operations
- The most basic arithmetic operation is the **addition** of two binary digits
- When both augend and addend are equal to 1, the binary sum consists of two digits ($1+1=10$). The higher significant bit of this result is called a carry. This carry is added to the next higher order pair of significant bits.
- A **combinational circuit** that performs the **addition** of **two bits** is called a **half adder**.

Half Adder


- **Half adder** adds two binary bits so it requires **two inputs** and **two outputs**
 - $0+0=0$; $0+1=1$; $1+0=1$; $1+1=10$
- The input variable designate the augend and addend bit, the output variables produce the **sum** (S) and **carry** (C)
- The truth table for half adder is shown. The C output is 1 only when both inputs are 1. The S output represents the least significant bit of the sum

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Half Adder Expressions

- The simplified sum of products expressions are:
 - $S = x'y + xy'$
 - $C = xy$
- It can be implemented in **sum of products**. It can also be implemented with an **exclusive-OR** and an **AND** gate
 - $S = x \oplus y$
 - $S = (x+y)(x'+y')$
 - $S' = xy + x'y'$
 - $S' = C + x'y'$
 - $S = (C + x'y')'$
 - $C = xy$
 - $C = (x'+y)'$

Logic Diagram of Half Adder

 
 
$$\begin{aligned} \text{(a)} \quad S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$\begin{aligned} \text{(b)} \quad S &= x \oplus y \\ C &= xy \end{aligned}$$

Fig. 4-5 Implementation of Half-Adder

Full Adder

- A **full-adder** is a combinational circuit that forms the arithmetic **sum** of **three bits** (three input bits).

- Two of the input variables x , y represents the two significant bits to be added
- The third input z represents the carry bit from the previous lower significant position
- Two output bits are necessary designated by the symbol S for sum and C for carry

- When all input bits are 0, the output is 0
- The S output is equal to 1 when only one input is equal to 1 or when all three inputs are equal to 1
- The C output has a carry of 1 if two or three inputs are equal to 1

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Maps for Full Adder

		y			
		yz	00	01	11
x	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
		z			

$m_1 = 1$
 $m_2 = 1$
 $m_4 = 1$
 $m_7 = 1$

$$S = x'y'z + x'yz' + xy'z' + xyz$$

		y			
		yz	00	01	11
x	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
		z			

$m_3 = 1$
 $m_5 = 1$
 $m_7 = 1$
 $m_6 = 1$

$$C = xy + xz + yz$$

Simplified Expressions for Full Adder

- The **simplified expressions** for **full adder** are

$$- S = x' y' z + x' y z' + x y' z' + x y z$$

$$- C = xy + xz + yz$$

 


Fig. 4-7 Implementation of Full Adder in Sum of Products

Full Adder with Two Half Adders

- Full adder can also be implemented with two half adders and an OR gate. The S output from the second half adder is the exclusive-OR of z and the output of the first half adder giving

$$- S = z \oplus (x \oplus y)$$


$$= z'(xy' + x'y) + z(xy' + x'y)'$$

$$= z'(xy' + x'y) + z(xy + x'y')$$

$$= xy'z' + x'yz' + xyz + x'y'z$$

$$- C = z(xy' + x'y) + xy$$

$$= xy'z + x'yz + xy$$

 

Binary Adder

- A **binary adder** is a digital circuit that produces the arithmetic **sum** of **two binary numbers**.
- A **binary adder** can be implemented using **multiple full adders** (FA) connected in cascade with the output carry from each full adder to the input carry of the next full adder in the chain

 


Fig. 4-9 4-Bit Adder

Binary Adder

- The augend bits of A and the addend bits of B are designated by subscript numbers from right to left, with subscript 0 denoting the least significant bit
- The carries are connected in a chain through the full adders
- The S outputs generate the required sum bits

<i>Subscript i:</i>	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Binary Adder

- Consider the two binary numbers, $A = 1011$ and $B = 0011$
- Their sum $S = 1110$ is formed with four-bit adders
- The bits are added with full adders, starting from the least significant position (subscript 0), to form the sum bit and carry bit
- The input carry C_0 in the least significant position must be 0
- The value of C_{i+1} in a significant position is the output carry of the full adder
- This value is transferred into the input carry of the full adder that adds the bits one higher significant position to the left

Subscript i	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Binary Adder

- The sum bits are thus generated starting from the rightmost position and are available as soon as the corresponding previous carry bit is generated
- All the carries must be generated for the correct sum bits to appear at the outputs

Subscript i	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Binary Adder

- A **binary adder** is a digital circuit that produces the arithmetic **sum** of **two binary numbers**.
- A **binary adder** can be implemented using **multiple full adders** (FA) connected in cascade with the output carry from each full adder to the input carry of the next full adder in the chain

 


Fig. 4-9 4-Bit Adder



The End